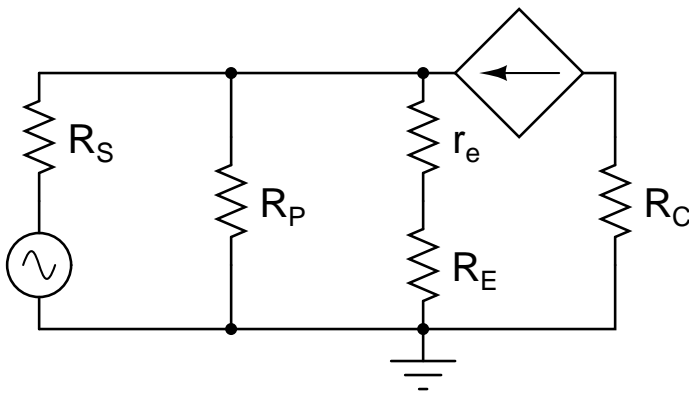



9.9

active: $v_{BE} = 0.7V, i_C = h_{FE}i_B$ KVL: $10V = 150k\Omega i_{B1} + 0.7V + 1k\Omega i_{B1}(1 + 100) \Rightarrow i_{B1} = \frac{9.3V}{251k\Omega} = 37.1\mu A = I_{BQ1} \Rightarrow I_{CQ1} = 3.71mA$ KVL: $10V = 1k\Omega(3.7mA + i_{B2}) + 0.7V + 1k\Omega i_{B2}(1 + 100) \Rightarrow i_{B2} = \frac{5.59V}{102k\Omega} = 54.8\mu A = I_{BQ2} \Rightarrow I_{CQ2} = 5.48mA$ KVL $\rightarrow V_{CEQ1} = 2.49V > 0.2V$ qedKVL $\rightarrow V_{CEQ2} = 2.66V > 0.2V$ qed

9.13

a.) $g_m = I_{CQ}/V_T = 1.18mA/26mV = 45.4mMHO$ b.) $r_e = V_T/I_{CQ} = 22\Omega$ c.) $R_P = R_1 R_2 / (R_1 + R_2) = 9k\Omega$. $R_b = v_b/i_b$ and $v_b = (r_e + R_E)101i_b \Rightarrow R_b = 103k\Omega$. R_{in} is now the parallel resistance of R_b and R_P : $R_{in} = 8.28k\Omega$ d.) With v_b as above and $v_c = -5k\Omega 100i_b$ we get: $A_v = v_c/v_b = -4.84$

9.18

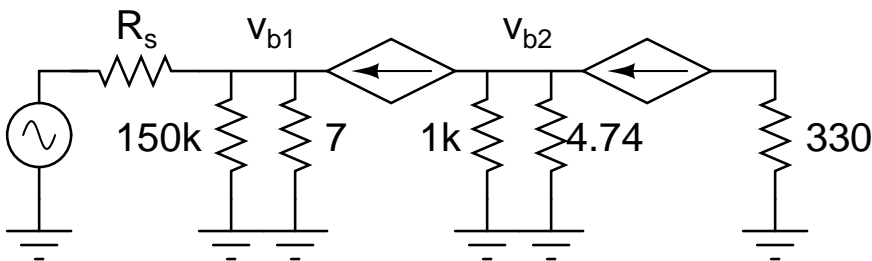


$$I_{CQ1} = 3.71\text{mA} \Rightarrow r_{e1} = 7 \text{ and } I_{CQ2} = 5.48\text{mA} \Rightarrow r_{e2} = 4.74$$

$$\text{a.) } v_{b1} = 7i_{b1}(1 + 100) \Rightarrow i_{b1} = v_{b1}/707 \text{ and } v_{b2} = 4.74i_{b2}(1 + 100) \Rightarrow i_{b2} = v_{b2}/479$$

$$100i_{b1} + v_{b2}/1k + i_{b2} = 0 \Rightarrow v_{b2} = -45.8v_{b1} \text{ and } v_{c2} = -330(100i_{b2}) = -330(100)(v_{b2}/479) \Rightarrow v_{c2}/v_{b1} = 3160 = A_v$$

$$\text{b.) } i_{c2} = -v_{c2}/330 \text{ and } i_{b2} = v_{b1}/707 \rightarrow i_{c2}/i_{b1} = -6770 = A_i$$

9.22

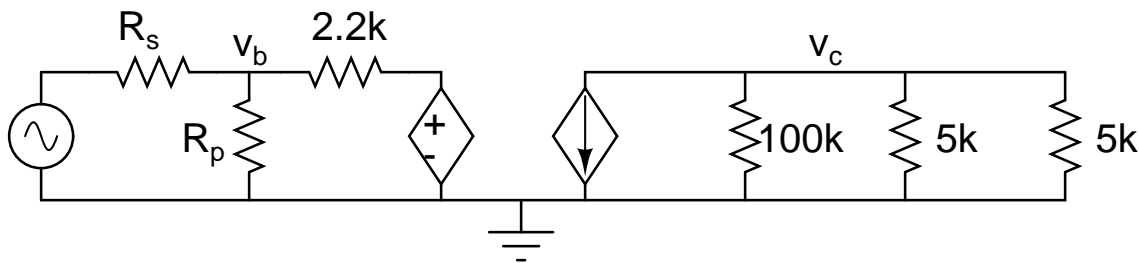

$$R_p = \frac{10k \cdot 90k}{10k + 90k} = 9k \text{ and } 100k || 5k || 5k = 2.44k$$

$$\text{a.) } i_b = \frac{v_b - 10^{-4}v_c}{2.2k} \text{ and } 100i_b + v_c/2.44k = 0 \Rightarrow i_b = -v_c/244k$$

$$-v_c/244k = (v_b - 10^{-4}v_c)/2.2k \Rightarrow v_c/v_b = 244 / -2.176 = -112 = A_v$$

$$\text{b.) } R_b = v_b/i_b = 2.18k \rightarrow R_{in} = R_b || R_p = 1.75k$$

$$\text{c.) } i_L = v_c/5k \Rightarrow i_L/i_b = -48.8 = A_i$$