

Write your name at the top right corner of every page (including this cover page).

Copy everything you want counted towards your grade onto the pages that I provided.

Write with a pen that cannot be erased!

No books are allowed!


Only the calculators I provided are allowed!

Write down all the steps that lead to your result.

Identify new variables that you may introduce in the circuit diagrams that I provided.

Read all the problems before you start so that you can begin with those that seem easiest to you.


MOSFET circuit symbols:

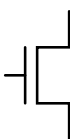enhancement mode MOSFET 

depletion mode MOSFET 

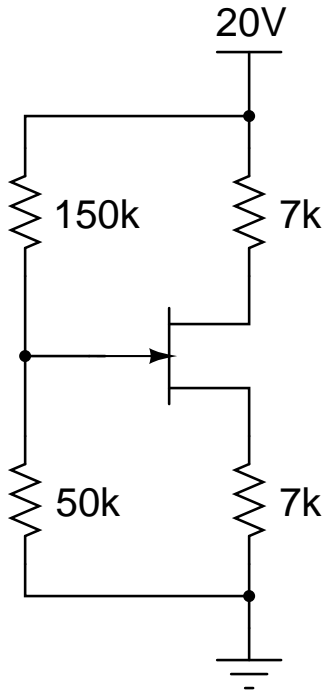**Problem 1 (6 pts):**

The JFET in the figure has  $I_{DSS} = 9 \text{ mA}$  and  $V_p = -3 \text{ V}$ . Find  $V_{GS}$ ,  $i_D$ , and  $V_{DS}$ .



$$V_G = \frac{50k}{50k+150k} 20V = 5V$$

$$i_D = I_{DSS}(1 - V_{GS}/V_p)^2 = 9m(1 + V_{GS}/3)^2 = 9m + 6mV_{GS} + 1mV_{GS}^2 = \frac{V_D}{7k} = \frac{V_G - V_{GS}}{7k} = (5 - V_{GS})/7k$$


$$\Rightarrow 7V_{GS}^2 + 43V_{GS} + 58 = 0 \Rightarrow V_{GS} = -2V (-4.14V < V_p)$$

$$i_D = \frac{5 - V_{GS}}{7k} = 1mA$$

$$V_{DS} = 20 - 2(7ki_D) = 6V$$

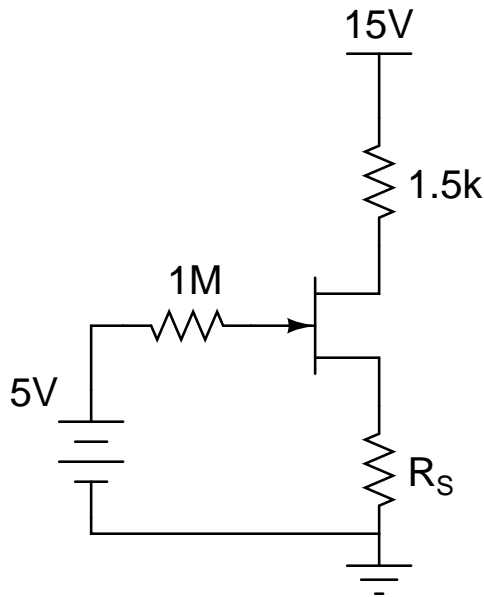**Problem 2 (6 pts):**

The JFET in the figure has  $I_{DSS} = 16 \text{ mA}$  and  $V_p = -2 \text{ V}$ . Find  $R_S$ ,  $V_{GS}$ , and  $V_{DS}$  so that the transistor is biased in the active (saturation) region (verify!) and  $i_D = 1 \text{ mA}$ .



$$i_D = I_{DSS}(1 - V_{GS}/V_p)^2 \Rightarrow \sqrt{i_D/I_{DSS}} = 1 - V_{GS}/V_p \Rightarrow V_{GS} = V_p(1 - \sqrt{i_D/I_{DSS}}) \Rightarrow V_{GS} = -1.5V$$


$$i_G = 0 \Rightarrow V_G = 5V; R_S = (V_G - V_{GS})/i_D = 6.5k\Omega$$

$$V_{DS} = 15 - (1.5 + 6.5)ki_D = 7V$$

$$V_{DS} > V_{GS} - V_p = 0.5V \text{ active region okay.}$$

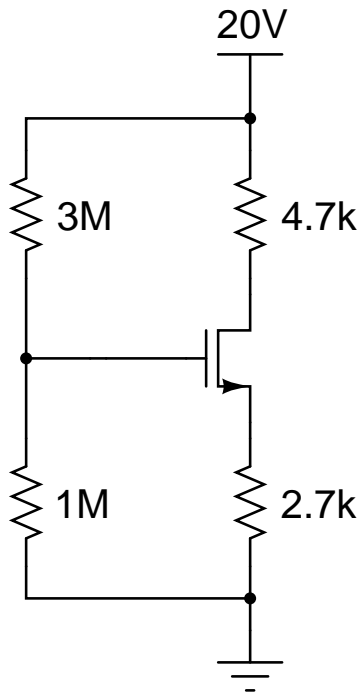**Problem 3 (6 pts):**

The NMOS in the figure has  $K = 1 \text{ mA/V}^2$  and  $V_t = 2 \text{ V}$ . Find  $V_{GS}$ ,  $i_D$ , and  $V_{DS}$ .



$$V_G = \frac{1M}{3M+1M}20 = 5V$$

$$V_G = V_{GS} + 2.7ki_D = V_{GS} + 2.7kK(V_{GS} - V_t)^2 \Rightarrow V_{GS}^2 - 3.63V_{GS} + 2.148 = 0 \Rightarrow V_{GS} = 2.886V (0.744V < V_t)$$

$$i_D = K(V_{GS} - V_t)^2 = 0.784mA$$


$$V_{DS} = 20 - (2.7 + 4.7)ki_D = 14.2V \Rightarrow \text{active region okay.}$$

**Problem 4 (7 pts):**


In the circuit below, the  $10\text{ k}\Omega$  resistor from  $v_{out}$  to GND represents the load resistance  $R_L$ . Draw the small signal equivalent circuit for this whole circuit. (including  $R_L$ )

Given  $g_m = 1.77\text{ mS}$ , what is  $A_v = v_{out}/v_{in}$ ? ( $r_d = \infty$ )

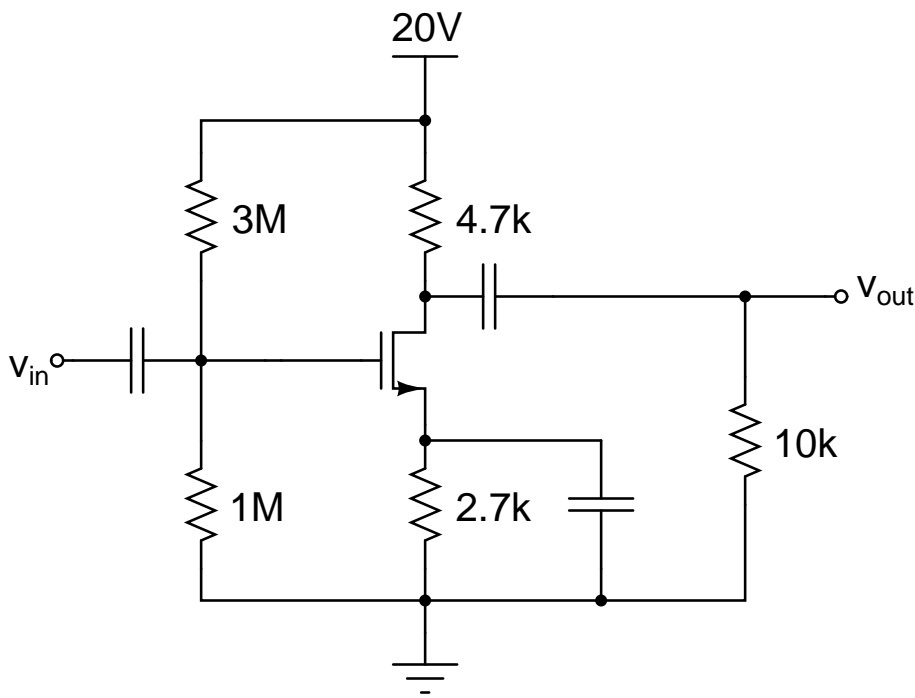Is the amplifier inverting or not? (check sign!)



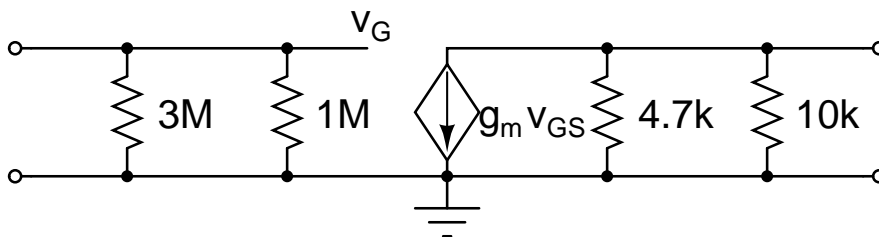The small signal equivalent circuit looks like this:




Since  $v_{in} = v_G = v_{gs}$  and  $v_{out} = v_d = -g_m v_{gs} \frac{4.7k \cdot 10k}{4.7k + 10k}$ , we get:

$$A_v = v_{out}/v_{in} = -g_m \frac{4.7k \cdot 10k}{4.7k + 10k} = -5.66$$

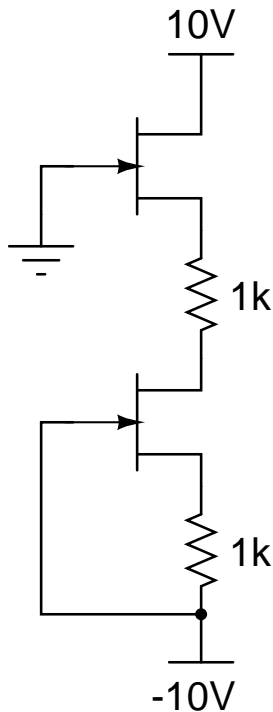**Problem 5 (7 pts):**

Both JFETs have  $I_{DSS} = 4 \text{ mA}$  and  $V_p = -2 \text{ V}$ . Assume active (saturation) region operation to find  $i_D$  and confirm that both JFETs are in the active region.



Let us give the index 1 to the lower JFET and index 2 to the upper JFET in the circuit drawing.

$$I_{DSS}(1 - V_{GS1}/V_p)^2 = i_D = 4m(1 + V_{GS1} + \frac{1}{4}V_{GS1}^2)$$

$$\text{Also: } i_D = V_S/1k = (-10 + V_{GS1})/1k \Rightarrow -V_{GS2}/1k = 4m(1 + V_{GS1} + \frac{1}{4}V_{GS1}^2)$$

$$\text{From } (V_{GS1} + 1)(V_{GS1} + 4) = 0 \text{ we get: } V_{GS1} = -1V (-4V < -2V = V_p)$$


$$i_D = -V_{GS1}/1k = 1mA$$

$$i_D/I_{DSS} = (1 - V_{GS2}/V_p)^2 \Rightarrow V_{GS2} = -1V \Rightarrow V_{S2} = 0 - V_{GS2} = 1V \Rightarrow (1V - (-10V)) = (1k + 1k)i_D + V_{DS1} \Rightarrow V_{DS1} = 9V > V_{GS1} - V_p = 1V, \text{ q.e.d.}$$

$$V_{DS2} = 10V - V_{S2} = 9V > V_{GS2} - V_p = 1V, \text{ q.e.d.}$$

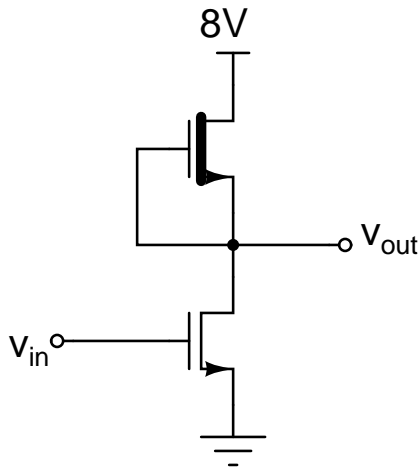**Problem 6 ONLY 6610 students !!! (7 pts):**

The MOSFETs below have the following characteristics:  $I_{DSS} = 4 \text{ mA}$  and  $V_p = -4 \text{ V}$  and  $K = 0.25 \text{ mA/V}^2$  and  $V_t = 1 \text{ V}$  respectively. What voltage will  $v_{in}$  have to be for both MOSFETs to be in the active region? What are  $i_D$  and  $v_{out}$  under these circumstances?



Let's give the index 1 to the lower MOSFET in the drawing and the index 2 to the upper one.

$$\text{Active, } V_{GS1} = V_{in} \text{ and } V_{GS2} = 0 \Rightarrow I_{DSS}(1 - V_{GS2}/V_p)^2 = i_D = K(V_{GS1} - V_t)^2 \Rightarrow v_{in} = 5V$$

$$V_{GS2} = 0 \Rightarrow i_D = I_{DSS} = 4mA$$

Check if active:

$$V_{DS1} \geq V_{GS1} - V_t = 4V \text{ and } V_{DS2} \geq V_{GS2} - V_p = 4V$$

$$\text{Also: } V_{DS1} + V_{DS2} = 8V \Rightarrow V_{DS1} = V_{DS2} = 4V$$