


Collab # 4 Solutions

Part 1 This can be approximated as a parallel plate capacitor

$$C = \epsilon_0 A/S = 8.85 \times 10^{-12} \frac{\pi (1)^2}{10^{-3}} = 2.78 \times 10^{-8} \text{ F}$$

Part 2 $U = \frac{1}{2C} Q^2 = \frac{1}{2} \frac{1}{2.78 \times 10^{-8}} (10^{-9})^2 = 1.8 \times 10^{-11} \text{ J}$

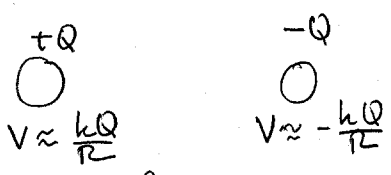
Part 3 To rough order of magnitude the answer should be the same as for spheres of radius $R=1\text{m}$. Consider charge $\pm Q$ on such spheres




$$\Delta V = \frac{2kQ}{R} \Rightarrow C = \frac{Q}{\Delta V} = \frac{R}{2k} = \frac{1}{18 \times 10^9}$$

$$\therefore C = 5.56 \times 10^{-11} \text{ F}$$

Part 4

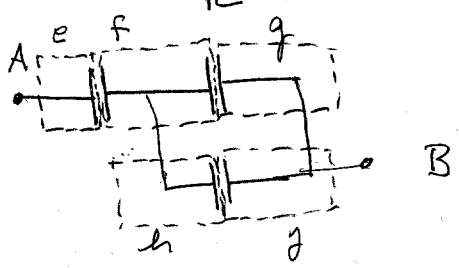


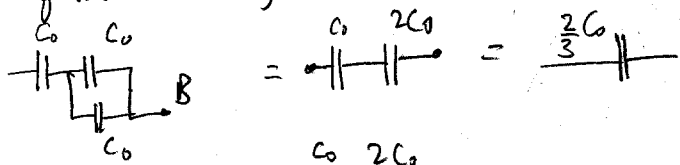part 5 Equivalent ckt, with $C_0 = 2.78 \times 10^{-8} \text{ F}$



$$C = \frac{2}{3} C_0 = \frac{2}{3} (2.78 \times 10^{-8} \text{ F}) = \boxed{1.85 \times 10^{-8} \text{ F}}$$

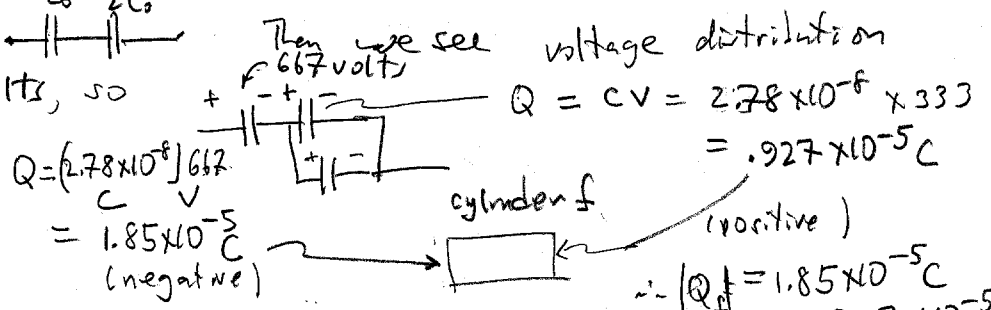part 6 View ckt as C_0 and $2C_0$ in series. is 667 volts and 333 volts, so



Prob 7 View it as $\frac{2}{3} C_0$ with 1000 volts


$$U = \frac{1}{2} CV^2 = \frac{1}{3} C_0 V^2 = \frac{1}{3} (2.78 \times 10^{-8}) (10^3)^2 = \boxed{9.27 \times 10^{-3} \text{ J}}$$

$$\therefore |Q_{\text{cyl}}| = 1.85 \times 10^{-5} \text{ C}$$

$$- .927 \times 10^{-5} \text{ C}$$

$$= \boxed{9.27 \times 10^{-6} \text{ C}}$$

Prob 8 without h we have

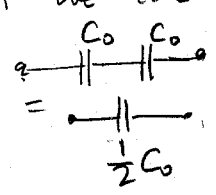

$$C = \frac{1}{2} C_0$$

The charge on the system is the same as in part 7

$$Q = \frac{2}{3} C_0 (1000 \text{ V}) = 1.85 \times 10^{-5} \text{ C}$$

$$\therefore U = \frac{1}{2C} Q^2 = \frac{1}{1C_0} Q^2 = 1.24 \times 10^{-2} \text{ J}$$

Thus work required = $\underbrace{1.24 \times 10^{-2} \text{ J}}_{U_{\text{without } h}} - \underbrace{9.27 \times 10^{-3} \text{ J}}_{U_{\text{with } h}} = \boxed{3.09 \times 10^{-3} \text{ J}}$