

SECOND EXAM

Name (Print) MOHAMMAD RAHI Name (Signed) M. Raahi


Discussion Instructor (Circle One): Cady McAllister Molina Stone

Discussion Section #: _____

SHOW ALL WORK!!!!
REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!
 Use the conversion constants and data given on the front page.


In the arrangement shown both switches are initially open and all capacitors are fully discharged. First, close S_1 with S_2 open. Then open S_1 , leaving S_2 open. Finally, close S_2 with S_1 still open. Work part (a) with the switches in this state. Capacitance values are without dielectric.

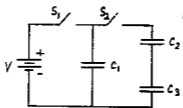- V = 110 V
- $C_1 = 7.25 \text{ pF}$
- $C_2 = 2.00 \text{ pF}$
- $C_3 = 5.00 \text{ pF}$




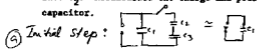(c) $V_1 = 91.93 \text{ volt} \approx 91.9 \text{ V}$
 $Q_1 = 6.66 \times 10^{-10} \text{ C}$
 $V_2 \approx 65.6 \text{ volt}$
 $V_3 \approx 26.3 \text{ volt}$
 $Q_2 = Q_3 = 1.31 \times 10^{-10} \text{ C}$

- 15 (a) Calculate the charge on and the potential difference across each capacitor.
 10 (b) With S_2 closed and S_1 open, as in (a), insert a dielectric with $\kappa = 5.00$, into C_2 . Recalculate the charge and potential difference for each capacitor.



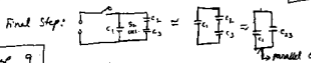C_1 is being charged
 $Q_1 = VC_1 = 7.925 \times 10^{-8} \text{ C} \approx 7.9 \times 10^{-8} \text{ C}$
 $\Rightarrow Q_{\text{TOT}} \text{ for } S_1 \text{-circuit.}$
 Since $C_{23} = \frac{C_2 C_3}{C_2 + C_3} = 1.43 \text{ pF}$



$C_{23} = \frac{C_2 C_3}{C_2 + C_3} = 1.43 \text{ pF}$
 $C_{23} = C_2 + C_3 = 8.68 \text{ pF}$

Set-up 9
 Answer 6

For parallel connection, both C_1 and C_{23} should have same p.d.
 $V_1 = P.D. \text{ in } C_1 = \frac{Q_{\text{TOT}}}{C_1} = V_{23} \Rightarrow \frac{7.98 \times 10^{-8} \text{ C}}{7.25 \times 10^{-12} \text{ F}} = \frac{Q_{23}}{8.68 \times 10^{-12} \text{ F}} = 91.93 \text{ volt}$
 $\therefore Q_1 = V_1 C_1 = 6.66 \times 10^{-10} \text{ C}$

Now $Q_T = Q_1 + Q_{23}$ where $Q_{23} = Q_2 = Q_3$ as C_2 & C_3 are in series.
 By conservation of charge, $Q_{23} = Q_1 = Q_2 \Rightarrow Q_T - Q_1 = 132.82 \times 10^{-12} \text{ C}$
 $= 1.33 \times 10^{-10} \text{ C}$

OVER

6 (a) Contd.

$$\therefore V_2 = \frac{Q_2}{C_2} = \frac{132.82 \times 10^{-12} \text{ C}}{2 \times 10^{-12} \text{ F}} = 66.41 \text{ Volt.}$$

$$= 66.4 \text{ Volt.}$$

$$V_3 = \frac{Q_3}{C_3} = \frac{132.82 \times 10^{-12} \text{ C}}{5 \times 10^{-12} \text{ F}} = 26.56 \text{ Volt} \approx 26.6 \text{ Volt.}$$

6

only C_2 will change in magnitude.

$$\text{Now, } C_2' = K C_2 = 5 \times 2 \times 10^{-12} \text{ F} = 1 \times 10^{-11} \text{ F}$$

Use $C_2' = 1 \times 10^{-11} \text{ F}$ in the equation of part (a) for C_2 .

$$\therefore C_{23}' = \frac{C_2' C_3}{C_2' + C_3} = \frac{10 \times 5}{15} \text{ pF} = 3.33 \times 10^{-12} \text{ F.}$$

$$\therefore C_{eq}' \Rightarrow C_1 + C_{23}' = (7.25 + 3.33) \times 10^{-12} \text{ F} \approx 10.58 \times 10^{-12}$$

$$\therefore V_1' = V_2' = \frac{7.98 \times 10^{-12}}{10.58 \times 10^{-12}} = \boxed{75.4 \text{ Volt.}}$$

$$Q_1' = V_1' C_1 = 75.4 \times 7.25 \times 10^{-12} = 546.65 \times 10^{-12} \text{ C.}$$

$$= \boxed{5.47 \times 10^{-10} \text{ C.}}$$

$$Q_2' = Q_3' = Q_T - Q_1' = \boxed{2.51 \times 10^{-10} \text{ C.}}$$

$$\therefore Q_T = 7.98 \times 10^{-10} \text{ C}$$

$$\therefore V_2 = \frac{Q_2'}{C_2'} = \frac{2.51 \times 10^{-10}}{10 \times 10^{-12}} = \boxed{25.1 \text{ Volt.}}$$

$$V_3 = \frac{Q_3'}{C_3} = \frac{2.51 \times 10^{-10}}{5 \times 10^{-12}} = 50.2 \text{ Volt.}$$

6 set up

4 ans +
Calc.