

Grader
 Name (Print) Pollard Name (Signed) _____

Discussion Instructor (Circle One): Brown Chung Pollard Rothman

Discussion Section #: _____ Schweizer Soderberg Vaseghi Viohl


REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!

Use the conversion constants and data given on the front page.

- (a) Calculate the effective capacitance between a and b. All capacitors have a value of 350 pF.

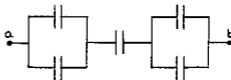175.0 pF

$$\frac{1}{C_T} = \frac{1}{2C} + \frac{1}{C} + \frac{1}{2C} = \frac{2}{C} \rightarrow C_T = \frac{C}{2}$$




- (b) In the circuit shown, the switch is closed for a long time. Calculate the voltage across the capacitor 250 s after the switch is opened.

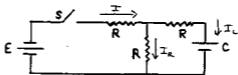66.6 Volts

See Solution on next page

- $\epsilon = 150 \text{ V}$
 $R = 350 \Omega$
 $C = 3.00 \text{ F}$




- (c) Silicon has an atomic mass of 28.0 and a density of $2.40 \times 10^3 \text{ kg/m}^3$. If a sample of silicon has a charge carrier density of $3.50 \times 10^{16} \text{ cm}^{-3}$, how many carriers per atom does it have?

$$\left(28 \frac{\text{g}}{\text{mole}}\right) \left(\frac{1 \text{ m}^3}{2.4 \times 10^3 \text{ g}}\right) \left(\frac{1 \text{ mole}}{6.02 \times 10^{23} \text{ atoms}}\right) \left(\frac{10^6 \text{ cm}^3}{\text{m}^3}\right)^3 (3.50 \times 10^{16} \frac{\text{carriers}}{\text{cm}^3}) = 6.78 \times 10^{-7} \frac{\text{carriers}}{\text{atom}}$$

- (d) Calculate the effective resistance between points a and b. All resistances are 7.00 ohm.

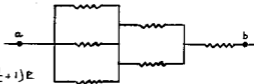12.83 Ω


$$R_T = \frac{1}{\frac{1}{2} + \frac{1}{2} + \frac{1}{2}} + \frac{1}{\frac{1}{2} + \frac{1}{2}} + R = \left(\frac{1}{3} + \frac{1}{2} + 1\right) R = \frac{11}{6} R$$



- (e) Calculate the voltage across the capacitor at $t = \infty$.

50.0 V

See Solution on next page

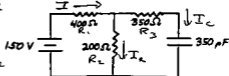

b) This can be done by realizing that the voltage across the capacitor as $t \rightarrow \infty$ is $\frac{\mathcal{E}}{2}$ or 75.00 Volts

and, for the discharging circuit, that $\tau = 2RC$.

$$\text{Then, } V(t=250s) = 75 e^{-250/1000} = 66.58 \text{ Volts.}$$

It can also be done by the "uninspired" method.

To do that, write down (i) junction equations,

(ii) loop equations, and (iii) $I_C = \frac{dQ}{dt}$, Then solve the resulting differential equation.

CHARGING CIRCUIT

$$\left. \begin{aligned} I &= I_R + I_C, \quad I_C = \frac{dQ}{dt} \\ I_R R - I_C R - Q/C &= 0 \\ \mathcal{E} - I R - I_R R &= 0 \end{aligned} \right\} \begin{array}{l} \text{for all } t \\ \text{in charging} \\ \text{circuit} \end{array}$$

putting together, we get

$$\frac{dQ}{dt} + \frac{2Q}{CR} = \frac{\mathcal{E}}{R}$$

the solution is .

$$Q(t) = [Q(t=\infty) - Q(t=0)] [1 - e^{-t/\tau}] + Q(t=0)$$

But we still need to calculate $Q(t=\infty)$ and $Q(t=0)$!

Note that $Q(t=\infty)$ will allow us to calculate what the voltage across the capacitor is when the switch is opened. We don't need the above D.E.!!

For $Q(t=\infty)$ note that $I_C \rightarrow 0$

We then have

$$\left. \begin{aligned} I &= I_R, \quad \frac{dQ}{dt} = 0 \\ I_R R - Q/C &= 0 \\ \mathcal{E} - I R - I_C R &= 0 \end{aligned} \right\} \begin{array}{l} \text{for } t = \infty \\ \text{in charging} \\ \text{circuit} \end{array}$$

From page
 solutions
 to b & c

b. cont) we then have

$$\mathcal{E} - I(R+R) = 0 \rightarrow I = \frac{\mathcal{E}}{2R}$$

$$IR - Q/C = 0 \rightarrow \frac{\mathcal{E}}{2} = \frac{Q}{C}$$

So the voltage across the capacitor as $t \rightarrow \infty$ is

$$V = \frac{Q}{C} = \frac{\mathcal{E}}{2} = 75.00 \text{ Volts}$$

DISCHARGING CIRCUIT (the switch is opened)
 no junction eq^s.



$$I(R+R) + Q/C = 0$$

$$I = \frac{dQ}{dt}$$

$$\rightarrow \frac{dQ}{dt} + \frac{Q}{2RC} = 0 \quad \therefore \tau = 2RC$$

The solution to this DE is $Q(t) = [Q(t=0) - Q(t=\infty)]e^{-t/\tau} + Q(t=\infty)$

here $Q(t=\infty) = 0$ & $Q(t=0)$ is the charge above

Since $V = \frac{Q}{C}$; $V(t) = \frac{Q(t=\infty)}{C} e^{-t/\tau} = (75.00 \text{ Volts}) e^{-t/\tau}$

So, $V(t=250 \mu\text{s}) = (75.00) e^{-250 \mu\text{s} / 100 \mu\text{s}} \text{ Volts} = 66.58 \text{ Volts}$

e) This can be done easily by realizing that for $t \rightarrow \infty$, the voltage across R_2 is equal to the voltage across the capacitor. for $t \rightarrow \infty$, $V_{R_2} = IR_2 = \mathcal{E} \frac{R_2}{R_1+R_2} = \mathcal{E} \left(\frac{1}{3}\right) = 50.0 \text{ Volts}$

$$\rightarrow V_C(t \rightarrow \infty) = 50.0 \text{ Volts}$$

The long way is just like charging circuit in part b), the difference being in the time constant as $R_1 \neq R_2 \neq R_3$

$$I = I_R + I_C \xrightarrow{t \rightarrow \infty} I = I_R = \frac{\mathcal{E}}{R_1+R_2}$$

$$I_R R_2 - I_C R_3 - Q/C = 0 \xrightarrow{t \rightarrow \infty} I_R R_2 = Q/C$$

Note: We don't need to calculate τ !

$$\frac{Q(t)}{C} = V(t) = [V(t=\infty)] (1 - e^{-t/\tau}) \xrightarrow{t \rightarrow \infty} V(t=\infty) = \frac{Q(t=\infty)}{C} = I_R R_2$$

$$V_C(t \rightarrow \infty) = \frac{\mathcal{E}}{R_1+R_2} R_2 = \mathcal{E} \frac{R_2}{R_1+R_2} = \frac{1}{3} \mathcal{E} = 50.0 \text{ Volts}$$