

THIRD MIDTERM

Name (print) David Nott Name (signed) \_\_\_\_\_

Discussion Instructor (circle): Condella Godfrey-Smith Guilkey Leong Nott Paul

Discussion Section # \_\_\_\_\_

**REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!**

**Use the conversion constants and data given on the front page.**

- (a) A copper rod, with circular cross section, has a radius of 1.200 cm. If it carries a current of 47,500 A, calculate the current density.

$$J = \frac{I}{A} = \frac{4.75 \cdot 10^4 \text{ A}}{\pi (1.2 \cdot 10^{-2} \text{ m})^2} = 1.050 \cdot 10^8 \frac{\text{A}}{\text{m}^2}$$

- (b) A 375 Ω resistor dissipates power at the rate of 4.40 Watts. Calculate the current.


$$P = I^2 R \quad I = \sqrt{\frac{P}{R}} = \sqrt{\frac{4.4}{375}} = .1083 \text{ A}$$

- (c) Calculate the equivalent capacitance between points A and B. All C's are 25 pf.

$$\frac{1}{\frac{1}{25} + \frac{1}{40}} = 15.38 \text{ pF}$$


~~25 + 25~~

- 25 in series with 25 → 12.5
- 12.5 in || with 25 → 37.5
- 37.5 in series with 25 → 15
- 15 in parallel with 25 → 40
- 40 in series with 25 → 15.38

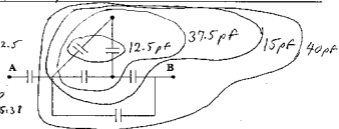

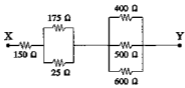- (d) Calculate the equivalent resistance between X and Y.

$$R_{eq} = 150 + \frac{1}{\frac{1}{25} + \frac{1}{175}} + \frac{1}{\frac{1}{400} + \frac{1}{500} + \frac{1}{600}} = 150 + 21.9 + 162 = 334 \Omega$$



- (e) Calculate the drift velocity for a current of 12,000 A in a copper rod with square cross section 1.00 cm on a side. Take the charge carrier density as  $6.00 \times 10^{29} \text{ m}^{-3}$ .

$$v_d = \frac{I}{nqA} = \frac{1.2 \cdot 10^4}{6 \cdot 10^{29} \cdot 1.6 \cdot 10^{-19} \cdot (1 \cdot 10^{-2})^2} \frac{\text{A}}{\text{C} \frac{\text{m}^2}{\text{m}^3}} = 1.250 \cdot 10^{-5} \frac{\text{m}}{\text{s}}$$