

THIRD MIDTERM

Name (print) Mikhail Portnoi Name (signed) _____

Discussion Instructor (circle): Basko Chakhbazian DiCarlo Gundlach Horner Wei




Discussion Section # _____

SHOW ALL WORK!!!!**REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!****Use the conversion constants and data given on the front page.**

For the circuit shown, and the values given, calculate:

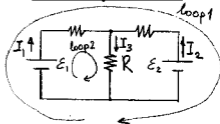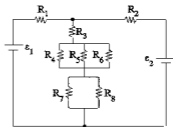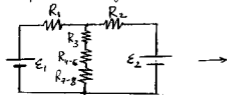- (a) the magnitude of the potential across R_1 ;
 (b) the magnitude of the potential across R_2 ;
 (c) the power being dissipated in R_5 ;
 (d) the power being dissipated in R_7 .

$$\begin{array}{ll} \epsilon_1 = 150 \text{ V} & \epsilon_2 = 100 \text{ V} \\ R_1 = 650 \Omega & R_2 = 350 \Omega \\ R_3 = 120 \Omega & R_4 = 50 \Omega \\ R_5 = 70 \Omega & R_6 = 80 \Omega \\ R_7 = 120 \Omega & R_8 = 80 \Omega \end{array}$$



$$1/R_{4-6} = 1/R_4 + 1/R_5 + 1/R_6 \Rightarrow R_{4-6} = 1/[1/50 + 1/70 + 1/80] = 21.4 \Omega$$

$$1/R_{7-8} = 1/R_7 + 1/R_8 = 1/80 + 1/120 \Rightarrow R_{7-8} = \frac{120 \cdot 80}{200} = 48 \Omega$$

$$R = R_3 + R_{4-6} + R_{7-8} = 120 + 21.4 + 48 = 189.4 \Omega$$

$$\text{Loop 1: } -\epsilon_1 + I_1 R_1 - I_2 R_2 + \epsilon_2 = 0$$

$$\text{Loop 2: } -\epsilon_1 + I_1 R_1 + I_3 R = 0$$

$$\text{Node: } I_1 + I_2 = I_3$$

$$\Rightarrow \begin{cases} I_2 = [I_1 R_1 - (\epsilon_1 - \epsilon_2)] / R_2 \\ I_1 R_1 + (I_1 + I_2) R = \epsilon_1 \end{cases} \Rightarrow$$

$$I_1 R_1 + \left(I_1 + \frac{I_1 R_1 - (\epsilon_1 - \epsilon_2)}{R_2} \right) R = \epsilon_1 \Rightarrow I_1 [R_1 R_2 + (R_1 + R_2) R] = \epsilon_1 R_2 + (\epsilon_1 - \epsilon_2) R$$

$$I_1 = \frac{\mathcal{E}_1 R_2 + (\mathcal{E}_1 - \mathcal{E}_2) R}{R_1 R_2 + (R_1 + R_2) R} = \frac{150 \times 350 + 50 \times 189.4}{350 \times 650 + 1000 \times 189.4} = 0.149 \text{ A}$$

$$I_2 = \frac{I_1 R_1 - (\mathcal{E}_1 - \mathcal{E}_2)}{R_2} = \frac{0.149 \times 650 - 50}{350} = 0.134 \text{ A}$$

$$I_3 = I_1 + I_2 = 0.283 \text{ A}$$

(a) $V_1 = I_1 R_1 = 0.149 \times 650 = 96.9 \text{ V}$

(b) $V_2 = I_2 R_2 = 0.134 \times 350 = 46.9 \text{ V}$

(or $V_2 = V_1 - (\mathcal{E}_1 - \mathcal{E}_2) = 96.9 - 50 = 46.9 \text{ V}$)

(c) $P_3 = I_3^2 R_3 = (0.283)^2 \cdot 120 = 9.61 \text{ W}$

(d) $P_7 = I_7^2 R_7$, where $I_7 R_7 = (I_3 - I_7) R_8 \Rightarrow$

$$\Rightarrow I_7 = I_3 \frac{R_8}{R_7 + R_8} \Rightarrow P_7 = R_7 \cdot (I_3)^2 \left(\frac{R_8}{R_7 + R_8} \right)^2 =$$

$$= 120 \cdot (0.283)^2 \left(\frac{80}{120 + 80} \right) = 1.54 \text{ W}$$