

THIRD MIDTERM

1

Name (print) Mike Hansen Name (signed) _____

Discussion Instructor (circle): Gramada Hansen Li Zhuok


Discussion Section # _____

REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!**Use the conversion constants and data given on the front page.**

- (a) Calculate the effective resistance between A and B if all resistors have the value of 30.0 ohms.




$$R_{eq} = \frac{14}{5} \Omega$$

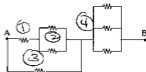

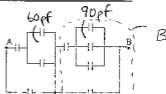- (b) Calculate the effective value of the capacitance between A and B if all capacitors have the value 30.0 pF.

$$B: \left[\frac{1}{90 \text{ pF}} + \frac{1}{30 \text{ pF}} \right]^{-1} \Rightarrow \frac{90}{4} \text{ pF} + 30 \text{ pF} = 52.5 \text{ pF}$$

$$A: \left[\frac{1}{60 \text{ pF}} + \frac{1}{30 \text{ pF}} \right]^{-1} + 30 \text{ pF} = 50 \text{ pF}$$



$$C_{eq} = \left[\frac{1}{50 \text{ pF}} + \frac{1}{52.5 \text{ pF}} \right]^{-1} = 25.6 \text{ pF}$$

- (c) If $\epsilon = 75.0 \text{ V}$, what is the power being dissipated in the 25 Ω resistor?

$$R_{eq} = 100 \Omega + 18.75 \Omega = 118.75 \Omega$$

$$V_{\text{Total}} = I_{\text{Total}} R_{eq} \Rightarrow I_{\text{Total}} = \frac{V_{\text{Total}}}{R_{eq}} = \frac{75 \text{ V}}{118.75 \Omega} = .632 \text{ A}$$


$$I_1 + I_2 = I_{\text{Total}} \quad V_1 = V_2 \Rightarrow V_1 = I_1 R_1 = I_2 R_2$$

$$V_1 = V_2 = I_{\text{Total}} R_2$$

$$= I_{\text{Total}} R_2 - I_1 R_2 \Rightarrow I_1 = \frac{I_{\text{Total}} R_2}{(R_1 + R_2)}$$

$$P_1 = V_1 I_1 = (11.85 \text{ V}) (0.474 \text{ A}) = 5.62 \text{ W}$$

$$= 4.74 \text{ W}$$

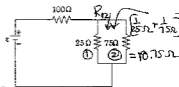

- (d) Calculate the drift velocity (in m/s) in a silver wire with current = 4.20 A that has a circular cross section with $r = 1.20 \times 10^{-3} \text{ m}$. Silver has $5.90 \times 10^{22} \text{ electrons/cm}^3$ that are mobile.

$$I = nq v_d A \Rightarrow v_d = \frac{I}{nqA} = \frac{4.20 \text{ A}}{5.9 \times 10^{22} \frac{e}{\text{cm}^3} \times 4 \times 10^{-8} \text{ m}^2} = 9.82 \cdot 10^{-5} \text{ m/s}$$

$$= \frac{5.9 \cdot 10^{20} \frac{e}{\text{m}^3} \times 1.609 \cdot 10^{-19} \text{ C} \times \pi \times (1.20 \cdot 10^{-3} \text{ m})^2}{4.20 \text{ A}} = 9.82 \cdot 10^{-5} \text{ m/s}$$

- (e) A parallel plate capacitor is constructed using a material whose dielectric constant is 4.27. If it is necessary to have the plate separator at 1.27 mm, what is the area needed to give $C = 17.0 \text{ pF}$?

$$C = K \epsilon_0 \frac{A}{d} \Rightarrow A = \frac{Cd}{K \epsilon_0} = \frac{17.0 \text{ pF} \cdot 1.27 \cdot 10^{-3} \text{ m}}{(4.27) (8.85 \cdot 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2})} = 5.71 \cdot 10^{-4} \text{ m}^2$$