

Name (print) Apostol Gramada Name (signed) \_\_\_\_\_

Discussion Instructor (circle): Gramada Hansen Li Zhukov

Discussion Section # \_\_\_\_\_

**SHOW ALL WORK!!!!****REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!****Use the conversion constants and data given on the front page.**

For the network shown,  $S_1$  is closed for a long time with  $S_2$  open.  $S_1$  is then opened and  $S_2$  closed.  $S_1$  remains open.

- (a) With  $S_2$  closed, find the potential on  $C_1$ .  
 (b) With  $S_2$  closed, calculate the charge on  $C_2$ .  
 (c) With  $S_2$  closed, what is the charge on  $C_2$ ?


$$V_{\text{batt}} = 120 \text{ V}$$

$$C_1 = 250 \text{ pF}$$

$$C_2 = 150 \text{ pF}$$

$$C_3 = 100 \text{ pF}$$

$$C_4 = 225 \text{ pF}$$

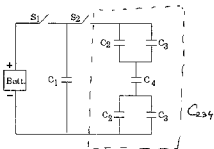

- a). The total charge after  $S_1$  is opened and  $S_2$  closed is:

$$Q = C_1 V_{\text{batt}} = \frac{30 \times 10^{-9} \text{ C}}{\sim 3 \text{ p.}}$$

$$C_{234} = \left( \frac{2}{C_2 + C_3} + \frac{1}{C_4} \right)^{-1} = 80.36 \text{ pF} \approx 80.4 \text{ pF}$$

$$C_{\text{eq}} = C_1 + C_{234} = 330.4 \text{ pF} \approx 330 \text{ pF} \sim 3 \text{ p.}$$

$$V_1 = Q / C_{\text{eq}} = \boxed{90.8 \text{ V}} \quad (10 \text{ p})$$

- b)  $Q_{23} = Q_2 + Q_3 = Q_4$ ;  $Q = Q_1 + Q_{23}$ ;  $Q_1 = V_1 C_1 = 2.27 \times 10^{-8} \text{ C}$

$$Q_4 = Q - Q_1 = (30 - 22.7) \times 10^{-9} = \boxed{7.30 \times 10^{-9} \text{ C}} \quad (5 \text{ p})$$

- c)  $Q_2 + Q_3 = 7.30 \times 10^{-9} \text{ C}$

$$\frac{Q_2}{C_2} = \frac{Q_3}{C_3}$$

$$\left. \begin{array}{l} \text{solve the} \\ \text{system} \end{array} \right\} \rightarrow \boxed{Q_2 = 4.38 \times 10^{-9} \text{ C}} \quad (10 \text{ p})$$

\* Credit was ~~not~~ given for meaningful work.