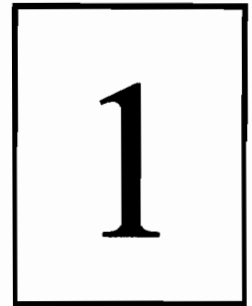


# THIRD MIDTERM



Name: \_\_\_\_\_ Student ID #: \_\_\_\_\_

Discussion Instructor (circle): Barcikowski      El-Gendy      Johnson      Rodriguez

**REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!**  
**Use the conversion constants and data given on the front page.**

- (a) Calculate the cyclotron frequency for electron in a magnetic field of 367 gauss (in Hz).

$\hookrightarrow 0.0367 \text{ T}$


$$f = \frac{qB}{2\pi m} = \frac{1.60 \times 10^{-19} \times 3.67 \times 10^{-2}}{2\pi \times 9.11 \times 10^{-31}} \approx 1.026 \times 10^9 \text{ Hz} \approx \boxed{1.03 \times 10^9 \text{ Hz}}$$

- (b) Calculate the drift velocity in a semiconductor with a carrier density of  $3.46 \times 10^{17}$  carriers/cm<sup>3</sup>. The current is 3.27 A in a wire with circular cross section and diameter 2.75 mm.

$\hookrightarrow 3.46 \times 10^{23} \text{ carriers/m}^3$   
 $\hookrightarrow 2.75 \times 10^{-3} \text{ m}$

$$V_D = \frac{I}{nqA} = \frac{3.27}{3.46 \times 10^{23} \times 1.60 \times 10^{-19} \times \pi \left(\frac{2.75}{2} \times 10^{-3}\right)^2} = 9.945 \approx \boxed{9.95 \text{ m/s}}$$

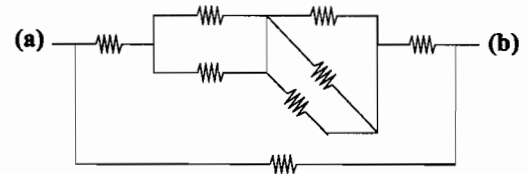- (c) All resistors have the same values,  $R = 100 \Omega$ . Calculate the effective resistance between (a) and (b). Numerical answer.



$$R + \frac{R}{2} + \frac{R}{3} + R = \frac{17}{6}R$$

$$\frac{6}{17}R + \frac{1}{R} = \frac{23}{17}R \Rightarrow \frac{17}{23}R = \frac{17}{23} \times 100 \Omega = 73.9 \Omega \approx \boxed{73.9 \Omega}$$


- (d) A 12.3 volt battery has an internal resistance of 0.75 ohm. What power will it deliver to an external load of 1.25 ohms?

$r_i$

$r_e$

$$I = \frac{\mathcal{E}}{r_i + r_e}, \quad P = I^2 r_e = \frac{\mathcal{E}^2 r_e}{(r_i + r_e)^2} = \frac{12.3^2 \times 1.25}{(0.75 + 1.25)^2} = 47.28 \text{ W} \approx \boxed{47.3 \text{ W}}$$

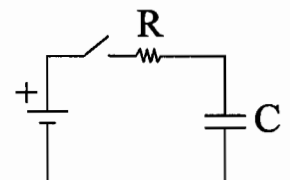- (e) Calculate the time constant for charging the capacitor if the resistor  $R = 17.500 \Omega$  and the capacitance is  $6.25 \mu\text{F}$ .



$\hookrightarrow 6.25 \times 10^{-6} \text{ F}$

$$\tau = RC = 17.5 \times 6.25 \times 10^{-6} = 1.094 \times 10^{-4} \text{ s} \approx \boxed{1.09 \times 10^{-4} \text{ s}}$$