

THIRD MIDTERM

3

Name: _____

Discussion Instructor (circle): Billeter Blake Herring Young


Discussion Section # _____

Student ID #: _____

SHOW ALL WORK!!!!
REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!
 Use the conversion constants and data given on the front page.

Initially S_1 is closed and S_2 is open.

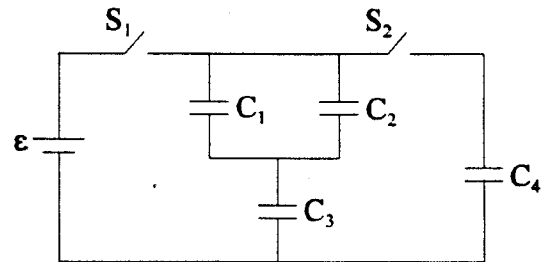- (a) [5 pts.] Calculate the effective capacitance for C_1, C_2, C_3 .
- (b) [5 pts.] Calculate the electric charge and potential on C_3 .
- (c) [7 pts.] Calculate the electric charge and potential on C_2 .



Now S_1 is opened and then S_2 is closed.

- (d) [8 pts.] Calculate the charge and potential on C_4 .

$\epsilon = 150 \text{ V}; C_1 = 2.0 \mu\text{F}; C_2 = 4.0 \mu\text{F}; C_3 = 5.0 \mu\text{F}; C_4 = 2.5 \mu\text{F}$


Solution:

(a) Initially S_1 is closed and S_2 is open. We can simplify the figure like this. Obviously, C_1 and C_2 is parallel. C_3 and C_1, C_2 is in series.

$$C_{12} = C_1 + C_2$$

$$C_{\text{effective}} = \left(\frac{1}{C_{12}} + \frac{1}{C_3} \right)^{-1} = \left(\frac{1}{C_1 + C_2} + \frac{1}{C_3} \right)^{-1}$$
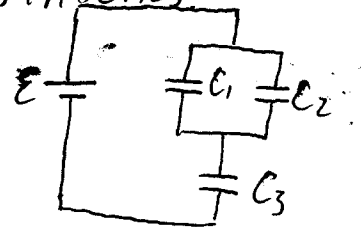
$$= \frac{C_3(C_1 + C_2)}{C_1 + C_2 + C_3}$$



$$= \frac{5.0 \mu\text{F} (2.0 \mu\text{F} + 4.0 \mu\text{F})}{2.0 \mu\text{F} + 4.0 \mu\text{F} + 5.0 \mu\text{F}} = \frac{30}{11} \mu\text{F} = \boxed{2.73 \mu\text{F}}$$

(b) $Q_{\text{effective}} = C_{\text{effective}} \cdot \epsilon$
 Because C_3 is in series.

$$V_3 = \frac{Q_3}{C_3} = \frac{4.09 \times 10^{-4} \text{ C}}{5.0 \times 10^{-6} \text{ F}} = \boxed{81.8 \text{ V}}$$

$$Q_3 = Q_{\text{effective}} = \boxed{4.09 \times 10^{-4} \text{ C}}$$

(c) $V_2 = V_{12} = \epsilon - V_3 = 150 \text{ V} - 81.8 \text{ V} = \boxed{68.2 \text{ V}}$


$$Q_2 = C_2 V_2 = 4.0 \mu\text{F} \cdot 68.2 \text{ V} = \boxed{2.73 \times 10^{-4} \text{ C}}$$

(d) Now S_1 is opened and S_2 is closed. We can simplify it. C_4 is charged. But total charge in the circuit is conserved.

$Q_{\text{total}} = Q_{\text{effective}} = 4.09 \times 10^{-4} \text{ C}$. C_4 and $C_{\text{effective}}$ is parallel.

$$Q_4 = C_4 V_4 = \boxed{1.96 \times 10^{-4} \text{ C}}$$
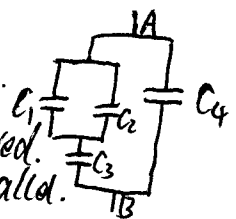
$$V_4 = V_{\text{total}} = \frac{Q_{\text{total}}}{C_{\text{total}}} = \boxed{78.2 \text{ V}}$$



THIRD MIDTERM

Problem 3. Grading Scale:

For all the question, if you have a wrong significant figure.
Subtract one point.

For part a, write correct effective capacitance formula, plus three points.
After correct calculation, get the final answer, plus 2 points.

For part b, write the formula $Q_3 = C_{\text{effective}} \cdot \mathcal{E}$, plus 2 points.
Get correct electric charge Q_3 , plus 1 points.
Write the voltage $V_3 = \frac{Q_3}{C_3}$ and then get correct answer
plus 2 points.

For part c, write $V_2 = \mathcal{E} - V_3$ or other similar formula and then
get the correct answer, plus 4 points.

Write $Q_2 = C_2 V_2$ and get the correct answer, plus 3 points.

For part d, write total charge in the circuit is conserved or
other similar description, plus 3 points.

Write effective capacitance $C_{\text{effective}}$ and C_4 is in
parallel, plus 3 points.

Get correct voltage on C_4 , plus 1 points.

Get correct charge on C_4 , plus 1 points.