

# FIFTH MIDTERM

# 4

Name: Weiran

Discussion Instructor (circle): Andrade      El-Gendy      Mimoto      Owen

Discussion Section # \_\_\_\_\_


Student ID #: \_\_\_\_\_

**SHOW ALL WORK!!!!**

**REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!**

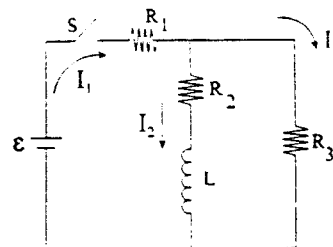**Use the conversion constants and data given on the front page.**


For the circuit shown, the switch S is closed at  $t = 0$  after being open for a long time.



- 5 (a) Just after  $t = 0$ , calculate the current in  $R_3$ .
- 5 (b) At  $t = \infty$  calculate the current in  $R_3$ .
- 5 (c) At  $t = \infty$  the switch is opened. Calculate the magnitude of the current in  $R_3$  1.5 time constants after the switch is opened.
- 10 (d) When the switch is closed at  $t = 0$ , calculate the time constant (numerical value) for the growth of current in the inductor. Use full loops and junctions with no short cuts. Use the current designations given.

$\epsilon = 150 \text{ V}; R_1 = 125 \Omega; R_2 = 175 \Omega; R_3 = 200 \Omega; L = 18.0 \text{ mH}$

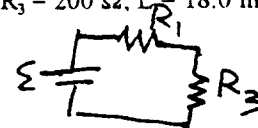(a) At  $t=0$ , No current flows through  $R_2$  and  $L$ ,



$$I_3 = \frac{\epsilon}{R_1 + R_3} = \boxed{0.462 \text{ A}}$$

(b) At  $t = \infty$ ,



$$I_3 = \frac{\epsilon}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}} \cdot \frac{R_2}{R_2 + R_3} = \boxed{1.32 \text{ A}}$$

$$I_1 = \frac{\epsilon}{R_1 + \frac{R_2 \cdot R_3}{R_2 + R_3}} = 0.687 \text{ A}$$

$$I_2 = I_1 - I_3 = 0.366 \text{ A}$$

(c)  $I = I_2 e^{-1.5\tau/\tau} = I_2 e^{-1.5} = \boxed{0.082 \text{ A}}$

(d)  $I_1 = I_2 + I_3$

$$\epsilon = I_1 R_1 + I_3 R_3$$

$$I_3 R_3 = I_2 R_2 + L \frac{dI_2}{dt}$$

$$\epsilon = I_2 R_1 + \frac{R_1 + R_3}{R_3} R_2 I_2 + \frac{R_1 + R_3}{R_3} L \frac{dI_2}{dt}$$

$$\frac{dt}{L \frac{R_1 + R_3}{R_3}} \cdot (R_1 + \frac{R_2 R_1}{R_3} + R_2) = - \frac{dI_2}{I_2 - \frac{\epsilon}{R_1 + \frac{R_2 R_1}{R_3} + R_2}}$$

$$\tau = \frac{L(R_1 + R_3)}{R_1 R_3 + R_1 R_2 + R_2 R_3} = \boxed{7.15 \times 10^{-5} \text{ s}}$$