

FINAL EXAM

3

Name: _____

Discussion Instructor (circle): Andrade El-Gendy Mimoto Owen

Discussion Section # _____

Student ID #: _____

3

SHOW ALL WORK!!!!

REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!

Use the conversion constants and data given on the front page.

An LC circuit includes a $30.0 \mu\text{F}$ capacitor and has a period of 2.50 ms . The peak value of the current is 13.0 mA .

- (a) Calculate the inductance in the circuit.
- (b) Calculate the peak value of the charge on the capacitor.

$$a) \quad \omega = 2\pi f = \frac{2\pi}{T} = \frac{1}{\sqrt{LC}} = \frac{2\pi}{2.5 \times 10^{-3}} = 2513 \text{ s}^{-1}$$

$$\therefore \frac{4\pi^2}{T^2} = \frac{1}{LC} \Rightarrow L = \left(\frac{T^2}{4\pi^2}\right) \frac{1}{C} = \frac{(2.5 \times 10^{-3})^2}{4\pi^2} \frac{1}{30 \times 10^{-6}} = 5.28 \text{ mH}$$

$$b) \quad I = \frac{dq}{dt} \Rightarrow I_p = \omega q_p$$

$$\Rightarrow q_p = \frac{I_p}{(2513)} = \frac{13 \times 10^{-3}}{2513} = 5.18 \text{ nC}$$