

FINAL EXAM

Name (print) _____ Name (signed) _____

Discussion Instructor (circle): Basko Chakhabzian DiCarlo Gundlach Romer Wei

Discussion Section # _____


SHOW ALL WORK!!!!

REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!


Use the conversion constants and data given on the front page.

Initially all capacitors are discharged.

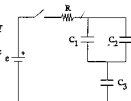- (a) If the switch is closed at $t = 0$, calculate the current in R as a function of time, evaluating all numerical constants.
- (b) After being closed a long time, the switch is opened, and then a dielectric with $\epsilon = 4.25$ is inserted in C_2 . Calculate the charge and potential on each capacitor after this event.
- (c) After (b) the switch is closed again. How much additional charge flows from the battery to the capacitors if you wait a long time?




$\mathcal{E} = 125 \text{ V}; C_1 = 850 \text{ pF}; C_2 = 275 \text{ pF}; C_3 = 400 \text{ pF}; R = 1.25 \times 10^6 \text{ Ohms}$

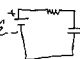(a)  $C_{\text{eff}} = \frac{(C_1 + C_2)C_3}{C_1 + C_2 + C_3} = \frac{2.79245 \times 10^{-10} \text{ F}}{1} = Q_{\text{charge}} = \frac{3.49056 \times 10^{-5} \text{ C}}{1}$

$i_R(t) = \frac{\mathcal{E}}{R} e^{-t/\tau} = 1 \text{ mA } e^{-\left[\frac{t}{3.49 \times 10^{-5} \text{ s}}\right]}$

Before insertion

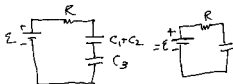


$\frac{(C_1 + C_2)C_3}{C_1 + C_2 + C_3} = C_{\text{eq}} \Rightarrow q_{\text{eq}} = C_{\text{eq}} \mathcal{E} = 3.4905 \times 10^{-8} \text{ C}$

$V_{3b} = 87.3 \text{ V}$
 $q_{3b} = 3.49 \times 10^{-8} \text{ C}$

$V_{2b} + V_{3b} = 37.7 \text{ V}$
 $\frac{q_{2b}}{825} + \frac{q_{3b}}{400} = 37.7 \text{ V}$
 $q_{2b} = 1.04 \times 10^{-8} \text{ C}$
 $q_{3b} = 2.45 \times 10^{-8} \text{ C}$

(b) After insertion

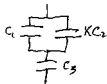

$\frac{C_3}{q_3 = 3.49 \times 10^{-8} \text{ C}}$	$\frac{C_2}{q_2 = 2.24 \times 10^{-8} \text{ C}}$	$\frac{C_1}{q_1 = 1.25 \times 10^{-8} \text{ C}}$
$V_3 = 87.3 \text{ V}$	$V_2 = 19.2 \text{ V}$	$V_1 = 19.2 \text{ V}$

(c)

$C_{\text{eq}} = 3.27887 \times 10^{-10} \text{ F}$
 $q_{\text{eq}} = 4.09859 \times 10^{-8} \text{ C}$

$\Rightarrow q_{\text{eq}} - q_{\text{eq, old}} = 6.08 \times 10^{-9} \text{ C}$