

FINAL EXAM

Name (print) ZHUKOV Name (signed) \_\_\_\_\_

Discussion Instructor (circle): Brown Chakhbazian Condella Portnoi Zhukov


Discussion Section # \_\_\_\_\_

**SHOW ALL WORK!!!!**

**REPORT ALL NUMBERS TO THREE SIGNIFICANT FIGURES!**

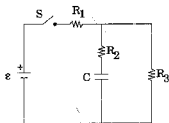**Use the conversion constants and data given on the front page.**

For the circuit shown the switch is open for a long time and then closed for exactly 2.00 time constants, and then opened.



- 8  
8  
14
- (a) Calculate the charge on the capacitor the instant the switch is opened.  
 (b) Find the magnitude of the current in  $R_3$   $6.00 \times 10^{-3}$  seconds after the switch is opened.  
 (c) As discussed in class, show in detail how to obtain the time constant for charging the capacitor and obtain a numerical value for that time constant.

$C = 2.40 \times 10^{-6} \text{ F}$   
 $\varepsilon = 225 \text{ V}$   
 $R_1 = 1.50 \times 10^3 \text{ ohms}$   
 $R_2 = 0.700 \times 10^3 \text{ ohms}$   
 $R_3 = 1.10 \times 10^3 \text{ ohms}$

For discharging  $Q(t) = Q_0 e^{-t/\tau}$ ,  $\tau = C(R_2 + R_3)$


$Q_0 = Q_{\infty} (1 - e^{-2})$ ,  $Q_{\infty} = \frac{C \varepsilon R_3}{R_1 + R_3}$

8 a)  $Q_0 = \frac{2.40 \times 10^{-6} \times 225 \times 1.1 \times 10^3}{1.5 \times 10^3 + 1.1 \times 10^3} (1 - e^{-2}) =$   
 $= 228.46 \times 10^{-6} (1 - 0.1353) = \underline{\underline{1.975 \times 10^{-4} \text{ C}}}$

8 b)  $\tau = 4.32 \times 10^{-3} \text{ s}$   $I(t) = I_0 e^{-t/\tau} = \frac{Q_0}{\tau} e^{-t/\tau}$   
 $t = 6.00 \times 10^{-3}$ ,  $I = \frac{1.98 \times 10^{-4}}{4.32 \times 10^{-3}} e^{-1.39} = \underline{\underline{1.14 \times 10^{-2} \text{ A}}}$

charging

c)

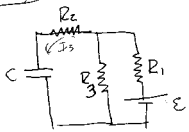

⊖ Missing  
Loop - source

$$\tau = C \left( R_2 + \frac{R_1 R_3}{R_1 + R_3} \right) = 2.4 \times 10^{-6} \left( 0.7 \times 10^{-3} + 0.655 \times 10^{-3} \right)$$

$$\tau = 3.20 \times 10^{-3} \text{ s}$$

\_\_\_\_\_